

Design of Bandgap Voltage Reference Circuits.

CTAT Voltage Generation Circuit

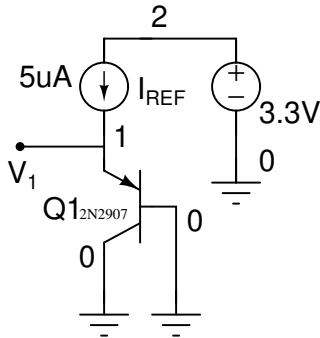


Figure 1: CTAT Generation Circuit

It can be observed that the voltage V_1 decreases with the increase in temperature T . Identify the slope $\partial V_1 / \partial T$ for the above circuit.

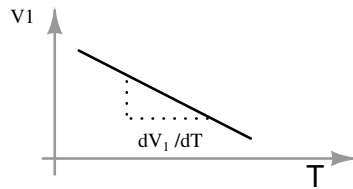


Figure 2: Variation of V_1 with temperature T

PTAT Voltage Generation Circuit

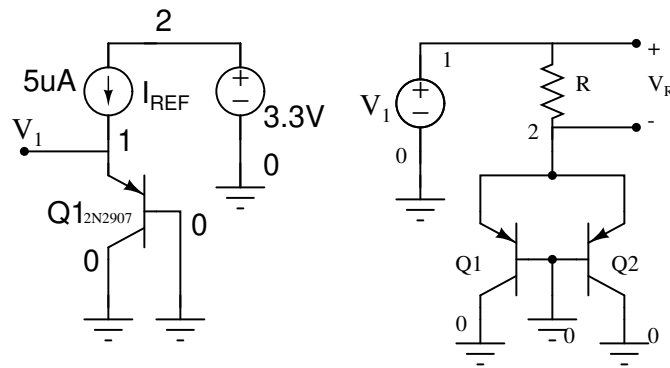


Figure 3: Basic PTAT Generation Circuit

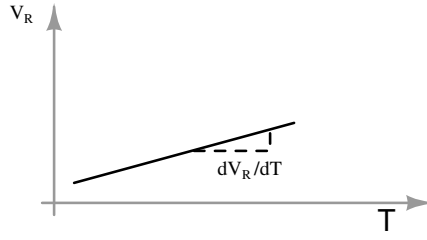


Figure 4: Variation of V_R with temperature T

It can be observed that the voltage V_R increases with the increase in temperature T . Identify the slope $\partial V_R / \partial T$ for the above circuit. Fig. 5 shows the PTAT Voltage generation with MOS current mirror.

$$V_R = V_T \ln(N) \quad (1)$$

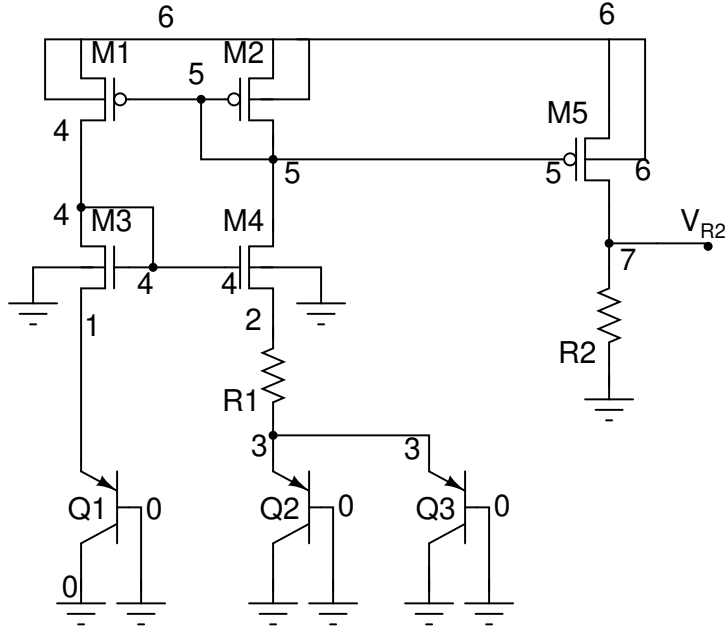


Figure 5: PTAT Voltage generation with MOS current mirror.

Design Exercise:

Design Bandgap voltage Reference circuit with $I_0 = 5\mu A$, $V_{DD} = 3.3 V$ and $N=2$.

From the Fig. 6, V_{REF} is expressed as,

$$V_{REF} = V_D + V_{R2} = V_D + (R_2/R_1)\ln(N)V_T \quad (2)$$

$$V_{REF} = \alpha_1 V_D + \alpha_2 V_T \quad (3)$$

On comparing Eq. 2 and Eq. 3

$$\alpha_1 = 1, \alpha_2 = (R_2/R_1)\ln(N).$$

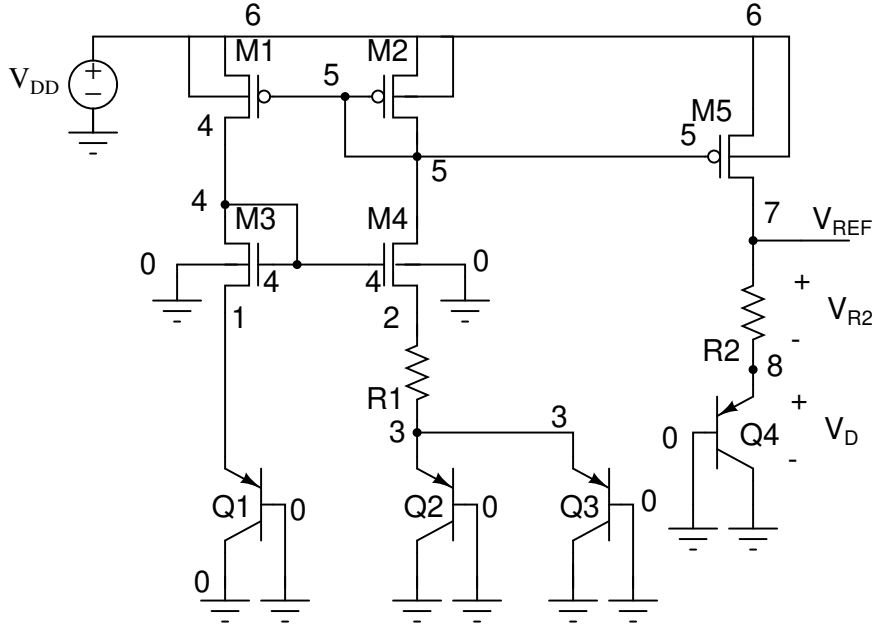


Figure 6: Voltage reference circuit with CTAT and PTAT combined.

For ZTAT behaviour of V_{REF} , it required to have

$$\frac{\partial V_{REF}}{\partial T} = \alpha_1 \frac{\partial V_D}{\partial T} + \alpha_2 \frac{\partial V_{R2}}{\partial T} = 0 \quad (4)$$

With $\alpha_1 = 1$, $\partial V_D / \partial T = -1.6 \text{ mV/K}$, $\partial V_T / \partial T = 86 \mu\text{V/K}$, $N=2$.

α_2 is evaluated to 17.44 and hence the relation between R_1 and R_2 is written as,

$$R_2 = 25.163 R_1 \quad (5)$$

Evaluation of R_1

The voltage across R_1 , V_{R1} is expressed as,

$$V_{R1} = I_o R_1 = V_T \ln(N) \quad (6)$$

With $I_o = 5 \mu\text{A}$, $V_T = 26 \text{ mV}$ [at $T=27^\circ\text{C}$], $N = 2$.

R_1 is evaluated to $3.6 \text{ K}\Omega$.

Evaluation of R_2

From Eq. 5, R_2 is evaluated to $90.5 \text{ K}\Omega$.

Exercise

1. Plot the voltages V_{R2} , V_D and V_{REF} . Observe the behaviour of these voltages with the variation in temperature.

2. Repeat 1 for different values of R_1 , R_2 and N .
3. Observe the behaviour of circuit with the variation in supply voltage V_{DD} .
4. Simulate the voltage reference circuit as shown in Fig. 7. Use previously designed opamp for the simulation.

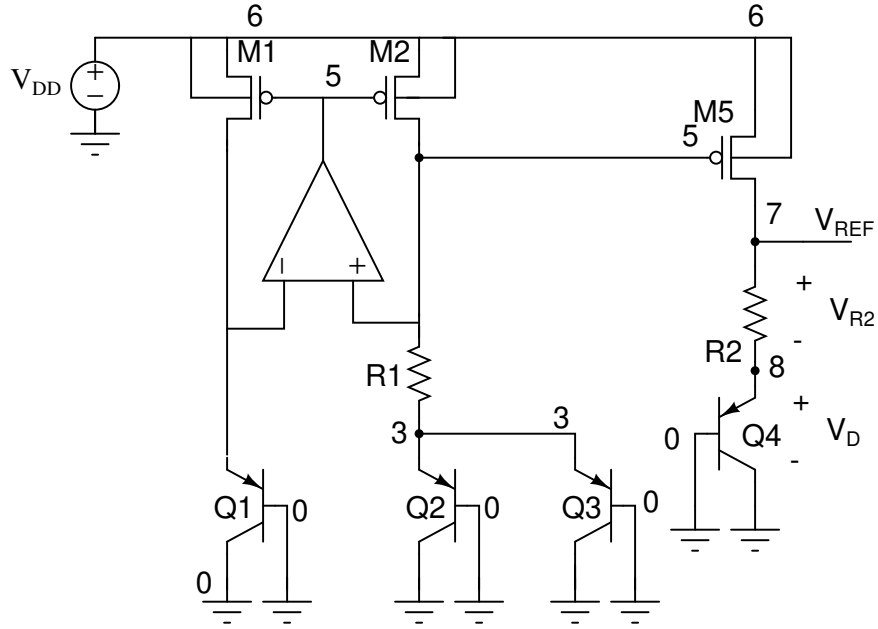


Figure 7: Voltage reference circuit with OPAMP.