

Layout for Differential Amplifier

- Write the SPICE for the differential amplifier shown in Fig. 1 and measure the dc gain.
- Draw the layout for the same and perform the post layout simulation.

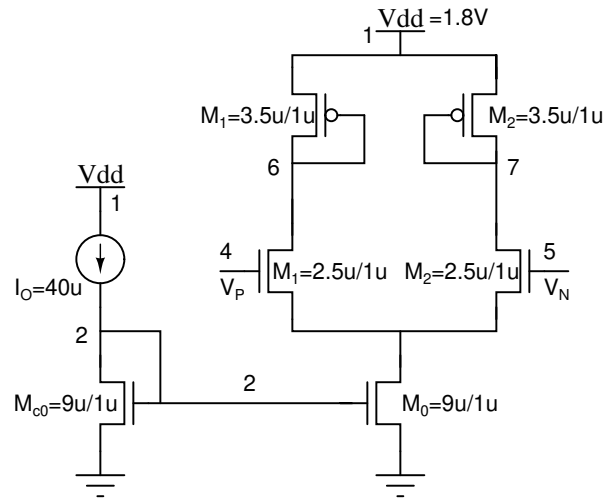


Figure 1: Differential Amplifier with diode connected load .

Exercise

Draw the layout for the latch shown in Fig. 3.

